


Variable Resistance



Fill in rectangle completely.
1. fill with vertical strokes
2. fill with horizontal strokes

A Switch

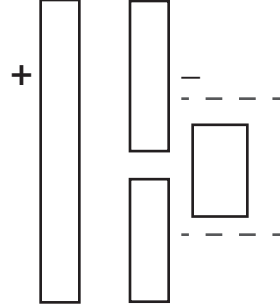Fill in the rectangles completely.
1. fill with vertical strokes
2. fill with horizontal strokes
3. cut along the dashed line




cut along dashed lines

cut along dashed lines

Flashlight

Fill in both paths completely.
1. fill with vertical strokes
2. fill with horizontal strokes

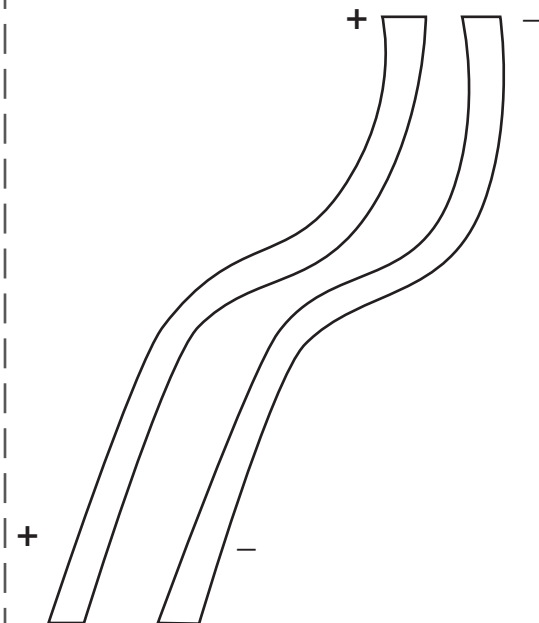Cut this section off.
by cutting along the dashed lines



Design your own circuit

cut along dashed lines

